 


Name \_\_\_\_\_

1. (6 points) Use DeMorgan's law to draw an equivalent gate representation of each of the following:



2. (6 points) An ASCII code table is provided below. Convert the hexadecimal numbers below, represented in ASCII code to their equivalent alpha- numeric representation.

**USASCII code chart**

Bits					Column	0	1	2	3	4	5	6	7
b <sub>7</sub>	b <sub>6</sub>	b <sub>5</sub>	b <sub>4</sub>	b <sub>3</sub>	Row	0	1	2	3	4	5	6	7
0	0	0	0	0	0	NUL	DLE	SP	0	@	P	\	p
0	0	0	0	1	1	SOH	DC1	!	1	A	Q	a	q
0	0	0	1	0	2	STX	DC2	"	2	B	R	b	r
0	0	0	1	1	3	ETX	DC3	#	3	C	S	c	s
0	0	1	0	0	4	EOT	DC4	\$	4	D	T	d	t
0	0	1	0	1	5	ENQ	NAK	%	5	E	U	e	u
0	0	1	1	0	6	ACK	SYN	&	6	F	V	f	v
0	0	1	1	1	7	BEL	ETB	'	7	G	W	g	w
0	1	0	0	0	8	BS	CAN	(	8	H	X	h	x
0	1	0	0	1	9	HT	EM	)	9	I	Y	i	y
0	1	0	1	0	10	LF	SUB	*	:	J	Z	j	z
0	1	0	1	1	11	VT	ESC	+	;	K	[	k	{
0	1	1	0	0	12	FF	FS	,	<	L	\	l	
0	1	1	0	1	13	CR	GS	-	=	M	]	m	}
0	1	1	1	0	14	SO	RS	.	>	N	^	n	~
0	1	1	1	1	15	SI	US	/	?	O	_	o	DEL

47	69	76	65	20	6D	65	20	61	6E	20	41	2E
G	i	v	e	[sp]	m	e	[sp]	a	n	[sp]	A	.

3. An 8 button keypad has a wireless transmitter that generates a 3 bit serial code for each key pressed. An additional parity bit is added before transmission so that the full 4 bit data block has odd parity. [Parity is defined as the number of 1's in a set of bits.]

- a. (4 points) Fill in the parity bit for each set of bits in the table below so that every 4 bit transmission will have odd parity:

<b>a</b>	<b>b</b>	<b>c</b>	<b>P</b>
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0



- b. (4 points) Write a Verilog statement using Sum of Products that generates the value of P:

```
P = (~a & ~b & ~c) | (~a & b & c) | (a & ~b & c) | (a & b & ~c);
```

- c. (4 points) Write a Verilog statement using XOR operators that generates the value of P:

```
P = ~(a ^ (b ^ c));
```

  4. (12 points) You are asked to expand the design of a 7 segment decoder in order to create a hexadecimal display, i.e., adding the symbols A,B,C,D,E,F to an existing Verilog design. The additional design information is given below (do not confuse the segment driver names (a-g) with the hexadecimal digits (A-F)). Write the Verilog code you would add to the design and indicate with an arrow where you would insert your code in the existing design.



```
4'b1010: seg_out = 7'b1110111;
4'b1011: seg_out = 7'b1111100;
4'b1100: seg_out = 7'b1011000;
4'b1101: seg_out = 7'b1011110;
4'b1110: seg_out = 7'b1111001;
4'b1111: seg_out = 7'b1110001;
```

```
module hex_decoder( input [3:0] hex_in,
                    output reg [6:0] seg_out );
    // seg_out maps bit 0 -> a ... bit 6 -> g
    ...
    always @ (hex_in) begin
        case (hex_in)
            4'b0000: seg_out = 7'b0111111;
            4'b0001: seg_out = 7'b0000110;
            4'b0010: seg_out = 7'b1011011;
            4'b0011: seg_out = 7'b1001111;
            4'b0100: seg_out = 7'b1100110;
            4'b0101: seg_out = 7'b1101101;
            4'b0110: seg_out = 7'b1111101;
            4'b0111: seg_out = 7'b0000111;
            4'b1000: seg_out = 7'b1111111;
            4'b1001: seg_out = 7'b1101111;
            default: seg_out = 7'b0000000;
        endcase
    end
    ...
```

5. (15 points) Design a digital circuit (a Verilog module) that provides a thermometer like readout using a string of 7 adjacent LED's, from a 3 bit binary input (unsigned integer). For example, if data\_in is equal to 0, all LED's are off; if data\_in is equal to 7, all 7 LED's are on; if data\_in is equal to 3, 3 adjacent LED's are on; ... so that the LED string behaves like viewing a thermometer. Assume that a logic one will turn on an LED. A control signal, ena is included. If ena is 0, the LED's are off; if ena is 1, the LED's are on. Start with the top module definition below. (I recommend using "case" and/or "if ... else" statements.)

```
module therm_code (input [2:0] data_in, input ena, output reg [6:0] led_array);
```

```
    always @ (ena, data_in) begin
        case (data_in)
            3'b000: led_array = 7'b00000000;
            3'b001: led_array = 7'b00000001;
            3'b010: led_array = 7'b00000011;
            3'b011: led_array = 7'b00000111;
            3'b100: led_array = 7'b00001111;
            3'b101: led_array = 7'b00011111;
            3'b110: led_array = 7'b00111111;
            3'b111: led_array = 7'b11111111;
            default: led_array = 7'b00000000;
        endcase
        if (ena === 0) led_array = 7'b00000000;
    end
```

```
endmodule
```


6. (12 points) Design a digital circuit (a Verilog module) that converts a 4 bit signed twos complement number into a 3 bit unsigned binary number (absolute value) with a sign bit (0 positive, 1 negative). (If you can't do this directly to Verilog, you should start with a truth table.)

```
module abs_val (input [3:0] d_2s_cmp, output reg [2:0] data_av, output reg sign);
```

```
    always @ (d_2s_cmp) begin
        case (d_2s_cmp)
            4'b1111: data_av = 1; // minus 1
            4'b1110: data_av = 2; // minus 2
            4'b1101: data_av = 3; // ...
            4'b1100: data_av = 4;
            4'b1011: data_av = 5;
            4'b1010: data_av = 6;
            4'b1001: data_av = 7; // minus 7
            default: data_av = d_2s_cmp[2:0]; // take care of positive
        endcase
        sign = d_2s_cmp[3]; // move the sign bit to sign
    end
```

```
endmodule
```

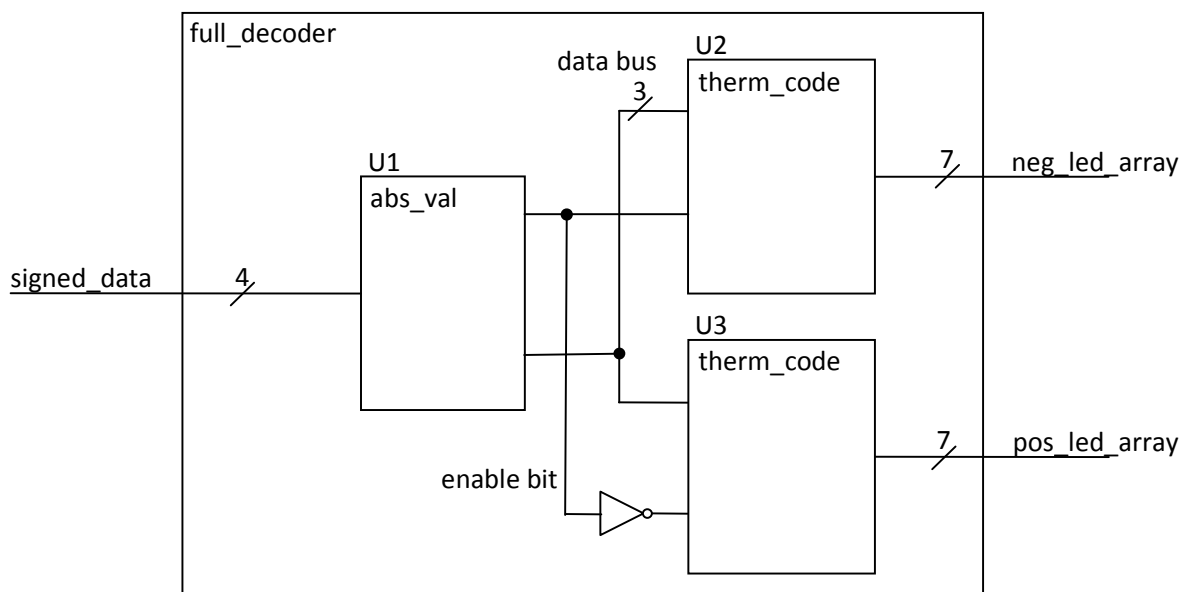7. (12 points) Using the modules defined in problems 5 & 6 (therm\_code, abs\_val), design the next level hierarchy illustrated in the block diagram below in a Verilog module. This module will now drive two sets of LED's, one set illuminated for positive numbers and the other for negative numbers.



```

module full_decoder (input [3:0] signed_data, output [6:0] pos_led_array,
                    output [6:0] neg_led_array);

    // define wire and reg variables
    wire [2:0] internal_d;
    wire internal_ena;
    wire internal_ena_bar;

    // use an assign statement to take care of inverted enable
    assign internal_ena_bar = ~internal_ena;

    // instantiate the three modules – I'll do the skeleton of the first one
    abs_val u1 ( signed_data, internal_d, internal_ena );

    therm_code u2 (internal_d, internal_ena, neg_led_array);

    therm_code u3 (internal_d, internal_ena_bar, pos_led_array);

endmodule

```