

Counter Integration

Vincent Martin
TUID: 913012274
ECE 2613
Lab #: 8 (10/22/2012)

Introduction:

The objective of this lab is to use our counters from lab 6 along with our display driver from lab 7 in order to create a counter block module that in this particular implementation, will be referred to as `ctr_blk`. Combining all of this functionality together will have the end result of being able to design a very rudimentary stopwatch/timer with limited functionality on to our Xilinx board.

This design will be accomplished by copying the code files from our previous labs and also instantiating new modules that we create from scratch, in particular a clock divider divide by 100 module that will set an output bit high for every count of 100.


Instantiation Applied to Our Design

The top level of our design will consist of the `sw_core` which inside will include an instantiation of the `dsp_drvr` which we will label as `udd`. This module was designed in our previous lab. For more understanding of this please refer to past labs.


Additionally, there will be another instance called `ucb` which will be of the `ctr_blk`. Inside of the `ucb` instance we will find yet more instantiations, this time called `u0`, `u1`, `u2`, `u3` and finally `u4`. These modules will all be of the `counter_0to9` type except for `u3`, which will be a `counter_0to5` variety and `u0` which will be an instantiation of `divideby100`.

Applying the Theory to Block Diagrams:

 
To best understand the modules that will be involved in our design it is good to look at block diagrams. Included below are block diagrams for our `divideby100` module, `ctr_block` and `sw_core`.



divideby100 block diagram

 

ctr_blk block diagram

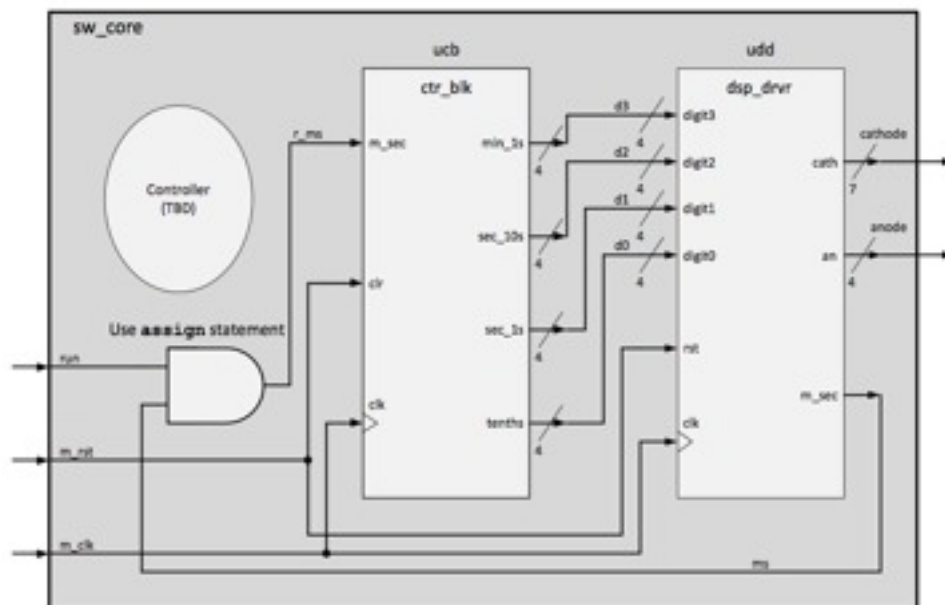

sw_core block diagram

Additionally we will want to implement a testing module. This scheme will utilize a .txt file, which will allow us to test all of our expected outcomes for our design.

Procedures:

Import the source code from previous labs

1. Connect to the design server using no machine
2. Execute XISE
3. Open the lab8 project in ~/xilinx/lab8
4. Add copies of the following files taken from your previous lab files
 - a. sw_core.v
 - b. dsp_drvr.v
 - c. svn_seg_decoder.v
 - d. 2612_lab7.ucf
 - e. counter_0to9.v
 - f. counter_0to5.v

Create the divideby100 module

1. Create a divideby100.v file using the new source wizard to give it the following input/output settings
 - a. input ena
 - b. input rst
 - c. input clk
 - d. output reg d_100
2. Create the logic that will cause d_100 be high every 100 count

Test the divideby100 module

1. Run iSim to check that there are no mis match errors
2. If there are errors correct the module

Create the ctr_blk module

1. Create a ctr_blk.v file using the new source wizard to give it the following input/output settings
 - a. input m_sec
 - b. input clr
 - c. input clk
 - d. output [3:0] tenths
 - e. output [3:0] sec_1s
 - f. output [3:0] sec_10s
 - g. output [3:0] min_1s
2. Define wires for chain 0, 1, 2 and 3.
3. Instantiate the following modules with the proper wire connections (See attached source for more details)

- a. divideby100 u0
- b. counter_0to9 u1
- c. counter_0to9 u2
- d. counter_0to5 u3
- e. counter_0to9 u4

Prepare sw_core

1. Instantiate the ctr_blk as ucb with all the proper connections (See attached source for more details)
2. Instantiate the dsp_drvr as udd with all the proper connections (See attached source for more details)
3. Create Wires with 3 bits called
 - a. d0
 - b. d1
 - c. d2
 - d. d3
4. Create a wire called ms
5. Create an assign statement of the following
 - a. "assign r_ms = run & ms"

Simulate the design

1. Navigate to the simulation mode
2. Launch iSim for the tb_sw_core
3. Run al simulation
4. Verify that the output works as expected (See results)

Compile to .bit file

1. Compile to a .bit file by navigating to
 - a. Implementation
 - i. Xc3s500-e4g320
 1. Lab7_top_io_wrapper (didn't rename)
 - a. Implement design
 - b. Generate programming file

Transfer .bit file to board

1. Use use your favorite network transfer program to move the .bit file from the development server to your local workstation
2. Plug the boar into the USB board
3. Launch Digilent Adept application
4. Click config tab
5. Click on browse by PROM icon
6. Select your .bit file
7. Click Program
8. Reset board to test

Results:

Below is iSim output from an input of the design simulation of tb_sw_core which appears to have worked properly and as expected.

Output from simulation of tb_sw_core:

iSim O.76xd (signature 0x8ddf5b5d)

This is a Full version of iSim.

WARNING: For instance udd/U1/, width 1 of formal port display_on is not equal to width 32 of actual constant.

Time resolution is 1 ps

Simulator is doing circuit initialization process.

Finished circuit initialization process.

iSim> run all

digit0 changed to: 1001111 - time: 100000020 ns
digit0 changed to: 0100100 - time: 200000020 ns
digit0 changed to: 0000110 - time: 200002020 ns
digit0 changed to: 0001011 - time: 200004020 ns
digit0 changed to: 0010010 - time: 200006020 ns
digit0 changed to: 0010000 - time: 200008020 ns
digit0 changed to: 1000111 - time: 200010020 ns
digit0 changed to: 0000000 - time: 200012020 ns
digit0 changed to: 0000010 - time: 200014020 ns
digit0 changed to: 1000000 - time: 200016020 ns
digit1 changed to: 1001111 - time: 200016040 ns
digit1 changed to: 0100100 - time: 200036040 ns
digit1 changed to: 0000110 - time: 200056040 ns
digit1 changed to: 0001011 - time: 200076040 ns
digit1 changed to: 0010010 - time: 200096040 ns
digit1 changed to: 0010000 - time: 200116040 ns
digit1 changed to: 1000111 - time: 200136040 ns
digit1 changed to: 0000000 - time: 200156040 ns
digit1 changed to: 0000010 - time: 200176040 ns
digit1 changed to: 1000000 - time: 200196040 ns
digit2 changed - to 1001111 - time = 200196060 ns
digit2 changed - to 0100100 - time = 200396060 ns
digit2 changed - to 0000110 - time = 200596060 ns
digit2 changed - to 0001011 - time = 200796060 ns
digit2 changed - to 0010010 - time = 200996060 ns
digit2 changed - to 1000000 - time = 201196060 ns
digit3 changed - to 1001111 - time = 201196080 ns
digit3 changed - to 0100100 - time = 202396080 ns
digit3 changed - to 0000110 - time = 203596080 ns
digit3 changed - to 0001011 - time = 204796080 ns
digit3 changed - to 0010010 - time = 205996080 ns
digit3 changed - to 0010000 - time = 207196080 ns
digit3 changed - to 1000111 - time = 208396080 ns
digit3 changed - to 0000000 - time = 209596080 ns

digit3 changed - to 0000010 - time = 210796080 ns
Simulation complete!!!

Results on board

Once the .bit file was transferred to the board I was able to see that I could reset and hold the counter. This works as expected.

Discussion:

This lab was exciting for me because it showed me in a more realistic way how all of our theory can be useful. Now we are left with a project that is more complete. I can now actually show someone that I made a partial stop watch which is pretty cool.

It was also interesting to note how the testing was completed in this lab. If we were to go ahead and test every permutation of the clock in the iSim simulator it would take a very long time. Instead we did a small hack so that the testing did not take as long. This is good that it saves us quite a bit of time.

Finally, as always, this lab allowed me to make quite a few mistakes and learn from them. The first mistake that cost me was that I accidentally made the wires 1 bit instead of 4 bit busses. This caused me all sorts of problems. Additionally I did not wire up all the modules correctly the first time. This also cost me some time. Surely this teaches me to be more careful in the future when I'm doing this sort of thing, especially with regards to design block diagrams.

Source Code:

ctr_blk.v

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 08:01:17 10/23/2012
// Design Name:
// Module Name: ctr_blk
// Project Name:
// Target Devices:
// Tool versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////
module ctr_blk(
    input m_sec,
    input clr,
    input clk,
    output [3:0] tenths,
    output [3:0] sec_1s,
    output [3:0] sec_10s,
    output [3:0] min_1s
);

//Wires!
wire chain0, chain1, chain2, chain3;

//Instantiations

divideby100 u0 (.ena(m_sec), .rst(clr), .clk(clk), .d_100(chain0));

counter_0to9 u1 (.ena(chain0), .clr(clr), .clk(clk), .carry_out(chain1), .q(tenths));
counter_0to9 u2 (.ena(chain1), .clr(clr), .clk(clk), .carry_out(chain2), .q(sec_1s));
counter_0to5 u3 (.ena(chain2), .clr(clr), .clk(clk), .carry_out(chain3), .q(sec_10s));
counter_0to9 u4 (.ena(chain3), .clr(clr), .clk(clk), .q(min_1s));

endmodule
```


counter_0to5.v

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 16:19:11 10/08/2012
// Design Name:
// Module Name: counter_0to5
// Project Name:
// Target Devices:
// Tool versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////
module counter_0to5(
    input ena,
    input clr,
    input clk,
    output reg [3:0] q,
    output reg carry_out);

//Declare reg for Next_q
reg [3:0] Next_q;

always @(posedge clk)
    begin
        q <= Next_q;
    end

    always @(q or ena or clr)
        begin

            Next_q = 4'b0000;
            carry_out = 4'b0;

            // ** HOLD **
            //Logic when ena and clr are set to 0 to hold current values
            if( (ena == 1'b0) && (clr == 1'b0))
                begin
                    carry_out = 1'b0;
                    Next_q[0] = q[0];
                end
        end
endmodule
```

```

        Next_q[1] = q[1];
        Next_q[2] = q[2];
        Next_q[3] = q[3];
    end

```

```

// ** MAX **
//Logic to handle when ena =1 and clr = 1 to get ouput
//of 5

```

```

if ( (ena ==1'b1) && (clr == 1'b1) )
    begin
        carry_out = 1'b1;
        Next_q = 4'b0101;
    end

```

```

// ** NEXT COUNT **
//Logic when ena = 1 to calculate our next bit

```

```

if ((ena == 1'b1) && (clr == 1'b0))
    begin

        Next_q = q + 1;

        if ( q == 5) carry_out = 1;
        if ( q >= 5) Next_q = 0;

    end // end of if handling the next bit

```

```

// ** CLEAR **
//Logic when clr = 1 and ena = 0 to clear
if ((clr == 1'b1) && (ena == 1'b0))
    begin

```

```

        Next_q = 4'b0000; // set to 0000.

```

```

        carry_out = 1'b0;

```

```

        // set the carry

```

```

    bit to 0.

```

```

    end // end if to set Next_1 and carry_out to 0.

```

```

end // End my entire always block

```

```

endmodule

```

counter_0to9.v

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 13:28:37 10/08/2012
// Design Name:
// Module Name: counter_0to9
// Project Name:
// Target Devices:
// Tool versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////
module counter_0to9(
    input ena,
    input clr,
    input clk,
    output reg[3:0] q,
    output reg carry_out
);

    //Declare Next_q reg type
    reg[3:0] Next_q ;

    //Let us do some logic on our input switches

    always @(posedge clk)
        begin
            q <= Next_q;
        end

    always @(q or ena or clr)
        begin

            Next_q = 4'b0000;
            carry_out = 4'b0;

            // ** HOLD **
            //Logic when ena and clr are set to 0 to hold current values
```

```

if( (ena == 1'b0) && (clr == 1'b0))
    begin
        carry_out = 1'b0;
        Next_q[0] = q[0];
        Next_q[1] = q[1];
        Next_q[2] = q[2];
        Next_q[3] = q[3];
    end

```

```

// ** MAX **
//Logic to handle when ena =1 and clr = 1 to get output
//of 9

```

```

if ( (ena ==1'b1) && (clr == 1'b1) )
    begin
        carry_out = 1'b1;
        Next_q = 4'b1001;
    end

```

```

// ** NEXT COUNT **
//Logic when ena = 1 to calculate our next bit

```

```

if ((ena == 1'b1) && (clr == 1'b0))
    begin

        Next_q = q + 1;

        if ( q == 9) carry_out = 1;
        if ( q >= 9) Next_q = 0;

    end // end of if handling the next bit

```

```

// ** CLEAR **
//Logic when clr = 1 and ena = 0 to clear
if ((clr == 1'b1) && (ena == 1'b0))
    begin
        Next_q = 4'b0000; // set to 0000.
        carry_out = 1'b0;
    end // end if to set Next_1 and carry_out to 0.

```

```

end // End my entire always block
endmodule

```

divideby100.v

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 13:50:10 10/22/2012
// Design Name:
// Module Name: divideby100
// Project Name:
// Target Devices:
// Tool versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////
module divideby100(
    input ena,
    input rst,
    input clk,
    output reg d_100
);

    // Register to store count and next count so that we can
    // count from 1 to 100 and then set d_100 to 1 every cycle.
    reg [0:7] count, next_count;

    // Sequential block
    always @(posedge clk) begin
        count <= next_count;
    end

    // Combinational block for count
    always @(ena, rst, count) begin

        // Default logic
        next_count = count;
        d_100 = 0;

        //Handle adding 1
        if ( ena == 1) begin
            next_count = count + 1;

            if ( count == 99) begin
```

```
                next_count = 0;  
                d_100 = 1;  
            end  
        end
```

```
    //Priority  
    if (rst == 1) begin  
        next_count = 0;  
    end
```

```
end // end of combinational block
```

```
endmodule
```

sw_core.v

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 14:14:01 10/12/2012
// Design Name:
// Module Name: sw_core
// Project Name:
// Target Devices:
// Tool versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////
module sw_core(
    input run,
    input m_rst,
    input m_clk,
    output [6:0] cathode,
    output [3:0] anode,
    output m_sec
);

//Wires and such
wire [3:0] d0, d1, d2, d3;
wire ms;
assign r_ms = run & ms;

//Instantiate the dsp_driver module as udd with kin of crazy format
//let us see that the spaces do not matter in this language.
dsp_drvr udd(
    .digit0(d0),
    .digit1(d1),
    .digit2(d2),
    .digit3(d3),
    .rst(m_rst),
    .clk(m_clk),
    .cath(cathode),
    .an(anode),
    .m_sec(ms));
```

```
ctr_blk ucb (  
    .m_sec(r_ms),  
    .clr(m_rst),  
    .clk(m_clk),  
    .min_1s(d3),  
    .sec_10s(d2),  
    .sec_1s(d1),  
    .tenths(d0));
```

```
endmodule
```


dsp_drvr.v

```
//
// lab7 : version 10/09/2012
//
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////

/////////////////////////////////////////////////////////////////
module dsp_drvr(
    input clk,
    input [3:0] digit0,
    input [3:0] digit1,
    input [3:0] digit2,
    input [3:0] digit3,
    input rst,
    output reg [3:0] an,
    output [6:0] cath,
    output reg m_sec
);

    // register for dividing by 50000
    reg [15:0] count, next_count;
    // register for anode control
    reg [1:0] anreg, next_anreg;
    // for multiplexed input into the decoder
    reg [3:0] mux_digit;
    // output from the decoder
    wire [6:0] seg_out;

    // sequential block
    always @(posedge clk) begin
        count <= next_count;
        anreg <= next_anreg;
    end // end of always block

    // combinational logic for count
    always @(count, rst) begin
        // take care of defaults
        next_count = count - 1;
        m_sec = 0;

        // normal logic
        if (count == 0) begin
            next_count = 49999;
            m_sec = 1;
        end
    end // priority logic
```

```

        if (rst == 1) next_count = 49999;
end    // end of count combinational logic

// anode control counter logic
always @(anreg, rst, m_sec) begin
    // defaults
    next_anreg = anreg;    // hold count
    // regular logic
    if (m_sec == 1) next_anreg = anreg + 1;
    // priority logic
    if (rst == 1) next_anreg = 0;
end    // end of anode combinational logic

// now do two muxes: digit mux and an signals
always @(anreg,digit0,digit1,digit2,digit3) begin
    an = 4'b1111;    // default
    case (anreg)
        0: begin
            mux_digit = digit0;
            an[3] = 0;
        end
        1: begin
            mux_digit = digit1;
            an[2] = 0;
        end
        2: begin
            mux_digit = digit2;
            an[1] = 0;
        end
        3: begin
            mux_digit = digit3;
            an[0] = 0;
        end
    endcase
end    // end of combinational mux

// finally instantiate the decoder here
svn_seg_decoder U1(.display_on(1), .bcd_in(mux_digit), .seg_out(seg_out));
assign cath = ~seg_out; // invert

endmodule

```

svn_seg_decoder.v

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 18:16:21 09/11/2012
// Design Name: seven segment decoder module
// Module Name: svn_seg_decoder
// Project Name: lab 03 seven segment decoder
// Target Devices: xilinx board
// Tool versions:
// Description: Take in 4 bits as a descriptor of the number you want to show and also
// 1bit as an on/off switch and then output the appropriate signal to drive
// the seven segment display.
//
// Dependencies:
//
// Revision: 2 (now using case statement)
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////
module svn_seg_decoder(
    input [3:0] bcd_in,
    input display_on,
    output reg [6:0] seg_out
);

// My always logic to replace old code
always @(display_on, bcd_in[3] or bcd_in[2] or bcd_in[1] or bcd_in[0]) begin

    case({display_on,bcd_in[3],bcd_in[2],bcd_in[1],bcd_in[0]})

        // Takes into account all combinations with the display turned off

        //Number 0000 Decimal Val: 0 Display: on *
        5'b10000: seg_out = 7'b0111111;

        //Number 0001 Decimal Val: 1 Display: on *
        5'b10001: seg_out = 7'b0110000;

        //Number 0010 Decimal Val: 2 Display: on *
        5'b10010: seg_out = 7'b1011011;

        //Number 0011 Decimal Val: 3 Display: on
        5'b10011: seg_out = 7'b1111001;

        //Number 0100 Decimal Val: 4 Display: on
```

```
5'b10100: seg_out = 7'b1110100;  
  
//Number 0101 Decimal Val: 5 Display: on  
5'b10101: seg_out = 7'b1101101;  
  
//Number 0110 Decimal Val: 6 Display: on  
5'b10110: seg_out = 7'b1101111;  
  
//Number 0111 Decimal Val: 7 Display: on  
5'b10111: seg_out = 7'b0111000;  
  
//Number 1000 Decimal Val: 8 Display: on  
5'b11000: seg_out = 7'b1111111;  
  
//Number 1001 Decimal Val: 9 Display: on  
5'b11001: seg_out = 7'b1111101;  
  
default: seg_out = 7'b0000000;
```

```
endcase
```

```
end
```

```
endmodule
```