

Weeks 3 & 4 Outline

- Multiple output SOP designs
- Verilog implementations
 - using SOP
 - using conditional statements
 - using case statements
- Logic operations on number systems
- More examples of combinational logic
- Exam 1 – Tuesday, Sept. 25th



Addition Tables

Decimal

+	0	1	2	3	4	5	6	7	8	9
0	0	1	2	3	4	5	6	7	8	9
1	1	2	3	4	5	6	7	8	9	0
2	2	3	4	5	6	7	8	9	0	1
3	3	4	5	6	7	8	9	0	1	2
4	4	5	6	7	8	9	0	1	2	3
5	5	6	7	8	9	0	1	2	3	4
6	6	7	8	9	0	1	2	3	4	5
7	7	8	9	0	1	2	3	4	5	6
8	8	9	0	1	2	3	4	5	6	7
9	9	0	1	2	3	4	5	6	7	8

Binary

+	0	1
0	0	1
1	1	0

Denotes Carry Operation



Addition Table for Hexadecimal

+	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
0	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
1	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F	0
2	2	3	4	5	6	7	8	9	A	B	C	D	E	F	0	1
3	3	4	5	6	7	8	9	A	B	C	D	E	F	0	1	2
4	4	5	6	7	8	9	A	B	C	D	E	F	0	1	2	3
5	5	6	7	8	9	A	B	C	D	E	F	0	1	2	3	4
6	6	7	8	9	A	B	C	D	E	F	0	1	2	3	4	5
7	7	8	9	A	B	C	D	E	F	0	1	2	3	4	5	6
8	8	9	A	B	C	D	E	F	0	1	2	3	4	5	6	7
9	9	A	B	C	D	E	F	0	1	2	3	4	5	6	7	8
A	A	B	C	D	E	F	0	1	2	3	4	5	6	7	8	9
B	B	C	D	E	F	0	1	2	3	4	5	6	7	8	9	A
C	C	D	E	F	0	1	2	3	4	5	6	7	8	9	A	B
D	D	E	F	0	1	2	3	4	5	6	7	8	9	A	B	C
E	E	F	0	1	2	3	4	5	6	7	8	9	A	B	C	D
F	F	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E

0 - denotes carry out is set



One Bit Addition (Half Adder)

- Arithmetically:
 $Z = A + B$
- Logically (Verilog):
 $Z = A \wedge B;$ (xor)
 $C = A \& B;$

Inputs		Outputs	
A	B	Z	C
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1



Multi-bit (Binary) Addition

- Compare to decimal addition

$$\begin{array}{r} 14 \\ + 7 \\ \hline 21 \end{array}$$

- Binary addition (expand to 5 bits)

$$\begin{array}{r} 11 \quad (\text{carries}) \\ 01110 \\ + 00111 \\ \hline 10101 \end{array}$$



Multi-bit (Binary) Addition (cont.)

- Addition examples:

$$Z = A + B;$$

Carry	0	1	1	0	1	1	1	x	Decimal
A	0	0	0	1	0	1	1	1	23
B	0	0	1	1	0	0	0	1	49
Z	0	1	0	0	1	0	0	0	72


Carry	1	1	1	1	0	1	1	x	Decimal
A	0	1	0	0	1	0	1	1	75
B	0	0	1	1	1	0	0	1	57
Z	1	0	0	0	0	1	0	0	132




One Bit Addition (Full Adder)

- Addition: $F = A + B$ (with carry)

Inputs			Outputs	
A	B	C _{in}	F	C
0	0	0	0	0
1	0	0	1	0
0	1	0	1	0
1	1	0	0	1
0	0	1	1	0
1	0	1	0	1
0	1	1	0	1
1	1	1	1	1

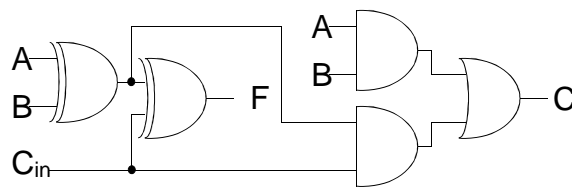

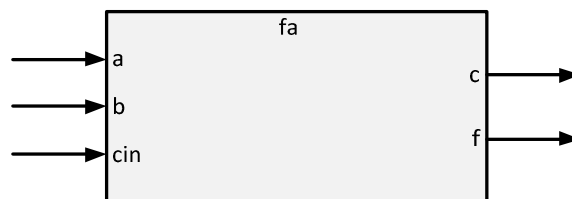Full Adder – Block Diagram & Verilog Module



```

module fa (a,b,cin,f,c);
  input a,b,cin;
  output f,c;
  ...
  ...
endmodule

```




Full Adder – Block Diagram & Verilog Module

- Implementation in class or as homework



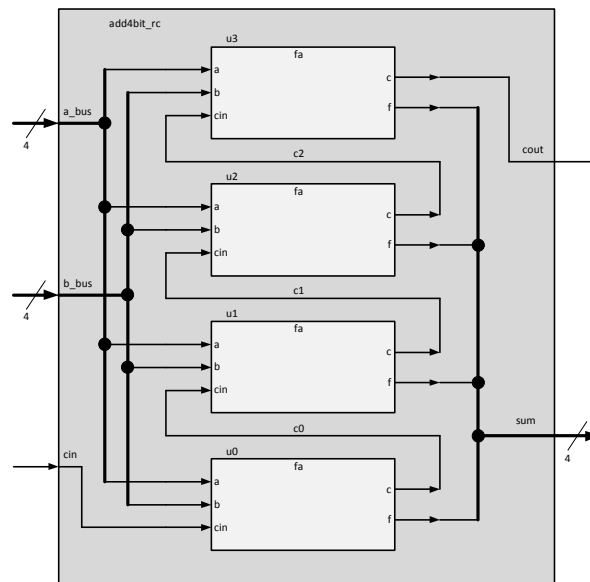Four Bit Adder Block Diagram (Ripple Carry)



Four Bit Adder Block Diagram (Ripple Carry)

- Implementation in class or as homework

```
module add4bit_rc (a_bus, b_bus, cin, sum, cout);  
    input [3:0]a_bus, b_bus;  
    input cin;  
    output [3:0]sum;  
    output cout;  
  
    // define the nets needed for interconnection  
  
    // instantiate the full adders  
  
    ...  
  
    ...  
endmodule
```



Signed Integers

- Binary numbers can represent both positive and negative values.
- For an n -bit number, there are still 2^n possible values, but now they are divided as half positive (including 0) and half negative.



Signed Integer Representations

- Signed magnitude: the most significant bit is used as the sign bit, e.g.:
 $3_{10} = 0011_2$ $-3_{10} = 1011_2$
- 1's complement: change 0's to 1's and 1's to 0's (C code symbol: ~)
 $3_{10} = 0011_2$ $-3_{10} = 1100_2$
- Many problems with both:
 - have two representations for 0
 - difficult to do simple binary arithmetic



Signed Integer Representations

- All processors use what is called 2's complement representation
- The conversion rule:
 - take the 1's complement of the binary number
 - add 1 to the binary number

$$3_{10} = 0011_2 \quad \sim 0011_2 = 1100_2 \quad -3_{10} = 1101_2$$



2's Complement Notation

- Example, 4 bit number:
 - 16 values
 - Unsigned: 0 to 15
 - Signed: -8 to +7
- One minor problem:
 - asymmetric in max & min values:
 - max: $2^{n-1} - 1$
 - min: -2^{n-1}

Value	Unsigned Integer	Signed Integer
0000	0	0
0001	1	1
0010	2	2
0011	3	3
0100	4	4
0101	5	5
0110	6	6
0111	7	7
1000	8	-8
1001	9	-7
1010	10	-6
1011	11	-5
1100	12	-4
1101	13	-3
1110	14	-2
1111	15	-1



2's Complement Notation

- A major advantage: arithmetic works seamlessly
 - addition
 - subtraction
- Examples:

2	0010	6	0110	-6	1010	5	0101
-2	1110	-2	1110	-2	1110	+2	0010
0	0000	4	0100	-8	1000	7	0111



2's Complement Sign Extension

- To extend a signed number from n bits to m bits:
 - add $m - n$ bits to the msb side
 - fill the extra bits with the value of the original msb
- Examples 4 bits to 8 bits:

Number	4 bit	8 bit
2	0 0 1 0	0 0 0 0 0 0 1 0
-2	1 1 1 0	1 1 1 1 1 1 1 0



2's Complement in Hexadecimal


- Same rules, but different symbols
 - find the complement (\sim) of each symbol
 - add 1 to the hexadecimal number

Hex Symbol	\sim (Hex Symbol)	\sim (Hex Symbol) + 1
0	F	0
1	E	F
2	D	E
3	C	D
4	B	C
5	A	B
6	9	A
7	8	9
8	7	8
9	6	7
A	5	6
B	4	5
C	3	4
D	2	3
E	1	2
F	0	1



Circular Representation of 2's complement, 4-bit numbers.

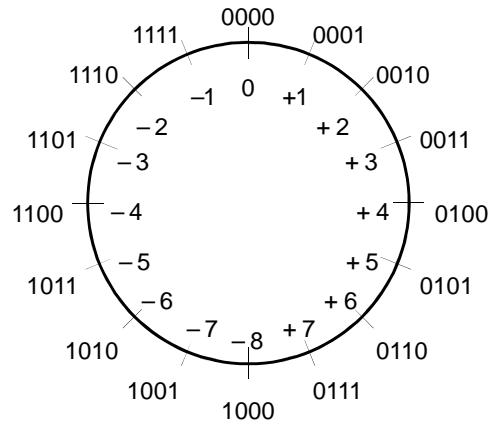- 4-bit range, 16 numbers: -8 to +7
- Clockwise for addition; CCW for subtraction



Parity

- Easiest implemented with XOR gates (remember our adders)
 - Example: 4 bit data to generate parity bit:
 $P = a[3] \oplus a[2] \oplus a[1] \oplus a[0];$ // for even
 $P = \sim(a[3] \oplus a[2] \oplus a[1] \oplus a[0]);$ // for odd
 - Data checking – 5 bit data checking bit:
 $check_bit = P \oplus a[3] \oplus a[2] \oplus a[1] \oplus a[0];$
- If even parity: check_bit should be 0
- If odd parity: check_bit should be 1



Gate Completeness

- For any Boolean function need: AND, OR, NOT
- What can be done with a NAND gate?
 - NOT operation:
 - Connect both inputs together
 - AND operation
 - Connect output of NAND to input of NOT
 - OR operation
 - Connect NOT's to inputs of NAND



Binary Addition (cont.)

- Addition – expressions

A/B/C_{in} result (carry)

$$0 + 0 + 0 = 0 \quad (0)$$

$$1 + 0 + 0 = 1 \quad (0)$$


$$1 + 1 + 0 = 0 \quad (1)$$

$$1 + 1 + 1 = 1 \quad (1)$$



Binary Arithmetic (cont.)

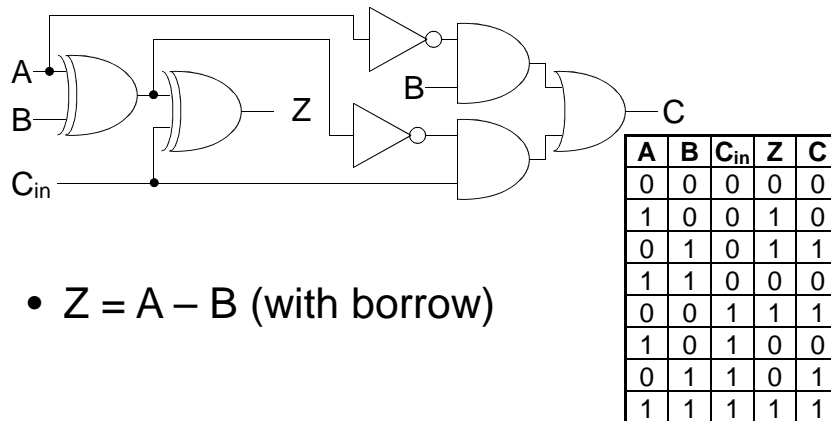- Subtraction (carry label is now a borrow)



- $Z = A - B$ (with borrow)



Binary Arithmetic

- Subtraction examples:

$$Z = A - B;$$

Carry	1	1	0	0	0	0	0	x	Decimal
A	0	0	0	1	0	1	1	1	23
B	0	0	1	1	0	0	0	1	- 49
Z	1	1	1	0	0	1	1	0	-26

Carry	0	1	1	0	0	0	0	x	Decimal
A	0	1	0	0	1	0	1	1	75
B	0	0	1	1	1	0	0	1	- 57
Z	0	0	0	1	0	0	1	0	18



Hexadecimal Arithmetic

- Use:
 - a) tables or
 - b) converting to decimal, and operating one digit at a time.
- Example of b):

$$Z = 0xBC4A + 0x3879$$

$$\dots$$

$$Z = 0xF4C3$$

Hex table

Carry	1	0	1	x
A	B	C	4	A
B	3	8	7	9
C	F	4	C	3

Decimal conversion

Carry	1	0	1	x
A	11	12	4	10
B	3	8	7	9
C	15	20	12	19
C mod 16	15	4	12	3



End of combinational logic lectures

- Review ... Exam 1

